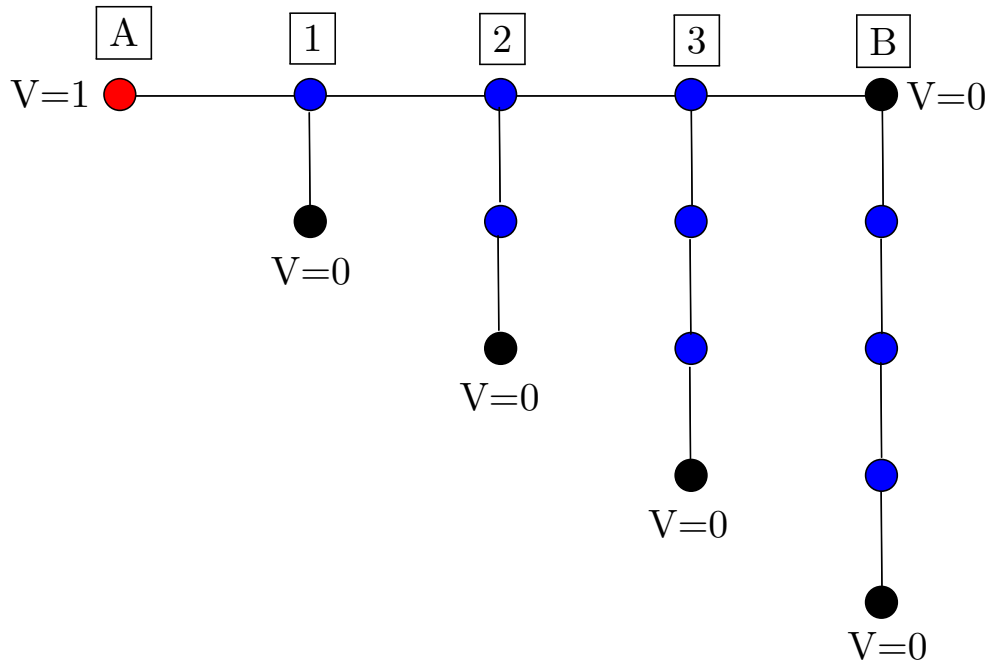


For maximum credit, **you must explain your answers clearly.**

All questions below relate to the following graph which is an electric circuit in which all edges have unit conductance:



Node  $\boxed{A}$  is set to unit voltage  $V = 1$ . There are 5 nodes that are grounded where the voltage  $V = 0$ , as indicated. Kirchhoff's current law holds at all other nodes.

- Without writing down the incidence matrix associated with the graph, find the rank of the incidence matrix and the dimension of its left nullspace.
- Determine the effective conductance between node  $\boxed{A}$  and the grounded nodes (that is, determine the net current out of node  $\boxed{A}$ ).
- Find the voltage at each of the nodes labelled  $\boxed{1}$ ,  $\boxed{2}$  and  $\boxed{3}$ .

THE END